 


The Von Neumann Architecture




John von Neumann
(December 28, 1903 – February 8, 1957)




- CPU – Central processing unit; the computer FSM.
- MEM – The memory; where **data** and **code** are stored.
- Dev – Devices; which digitize input signals and translates output signals.
- BUS – Bus for communication between components.

The Von Neumann Architecture

 

- Load data and code to the memory.
- Machine starts.
- The CPU reads code from the beginning of the memory and executes code until a HALT command is executed.


The Von Neumann Architecture

 

- Load data and code to the memory.
- Machine starts.
- The CPU reads code from the beginning of the memory and executes code until a HALT command is executed.




Design a specific machine according to this architecture.

The Von Neumann Architecture

 


- Code execution should allow branching and looping.

Modes of code execution

   

The Von Neumann Architecture

 

- The (input) device can **interrupt** the CPU code execution process, and put data to the memory. (e.g., key press)
- The CPU can call the (output) device to send data to it. (e.g., play sound)

Correspondingly, the following basic CPU functions are needed.

1. Loading data and tracking execution.
2. Arithmetic and logical functions.
3. Reading and writing memory.
4. Talking to devices.


How do we implement the above using circuit?

- Specify a computer word.
 - 32 bits = 4 bytes
 - communication, command, index
- Define the instruction set while designing the circuits.

1. Loading data and tracking execution.
2. Arithmetic and logical functions.
3. Reading and writing memory.
4. Talking to devices.

commands ↔ implementations


1. Loading and Executing Instructions

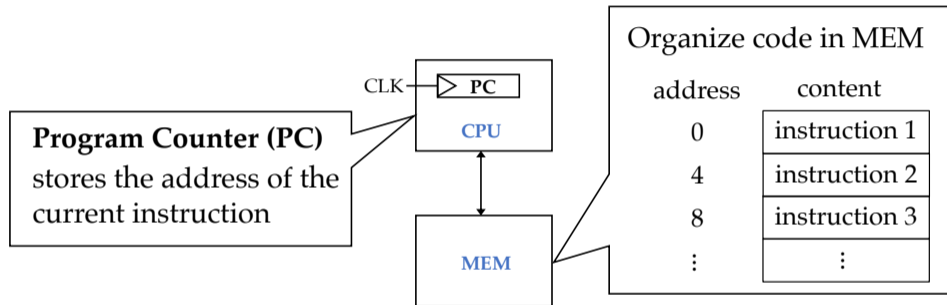

Why not 0, 1, 2 ?


byte addressing 1 word = 4 bytes

1. Loading and Executing Instructions

 

- **Program Counter (PC)**
stores the address of current instructions.
- **Control Unit (CU)**
interpret the current instructions.
- **Registers**
a small number of words for storing operands to compute.
- **Arithmetic Logical Unit (ALU)**
+ - × ÷ and or not ...

1. Loading and Executing Instructions

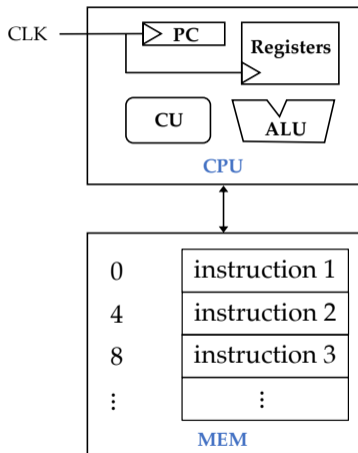

- Machine starts.
- PC starts from 0.


Repeat:

- Load a word (instruction) from PC address.
- CU interprets the instruction and sends signals to CPU components.
- PC increases by 4 or jumps according to CU instruction.


Until (HALT is the instruction):

- Machine stops.

1. Loading and Executing Instructions

 


2. Arithmetic and Logical Functions

 

- There are 32 registers, each being a computer word, to store data for computation hardware wiring.
- CPU operations are executed with registers, which contains operands and results for ALU, address for PC, etc.
- Why start with 0 (not 1) ? Binary encoding.

2. Arithmetic and Logical Functions

 

The operations

+ - × ÷ %

AND OR NOT

>> << ...

% — module


>>, << — shift

$$5 \% 2 = 1, 7 \% 4 = 3$$

$$00110010 \gg 2 = 00001100$$

$$00110010 \ll 3 = 10010000$$

2. Arithmetic and Logical Functions

 


The operations

+ - × ÷ %
AND OR NOT
>> << ...


- Are these enough for a computer ?
- Yes ! We learned $M \rightarrow N$ circuit and computation theory.

2. Arithmetic and Logical Functions

 


- The implementation
 - How to pack ALU instructions into a computer word?
 - How to wire the circuit?

2. Arithmetic and Logical Functions

 

- How to pack ALU instructions into a computer word?

32 bits

 


e.g.,

+	R26	R3	R4
---	-----	----	----

meaning adding the content of registers R3 and R4, and stores the result into register R26.

2. Arithmetic and Logical Functions

 

- How to pack ALU instructions into a computer word?

32 bits




➤ Allocate 6 bits to encode COMMAND.

- 000001 for +
- 000010 for -

...

- $2^6 = 64$ commands can be accommodated.

2. Arithmetic and Logical Functions

 

- How to pack ALU instructions into a computer word?

32 bits




➤ Allocate 5 bits to encode the registers for result and operand.

- 00000 for R0
- 00001 for R1
- 00010 for R2
- 00011 for R3
- ...
- 11111 for R31

✓ $2^5 = 32$ exactly



✓ binary index starts from 0

2. Arithmetic and Logical Functions

 

- How to pack ALU instructions into a computer word?

32 bits

  


$$26 = 16 + 8 + 2 = \text{binary } 11010$$

$\therefore R3 + R4 \Rightarrow R26$ is encoded in [000001101000011001000000000000]


This is what each instruction looks like!

2. Arithmetic and Logical Functions

 


- How to wire the circuits ?

Organize the registers into a component.

 

Knowledge in Chapters 3 and 4 allows us to build it.

2. Arithmetic and Logical Functions

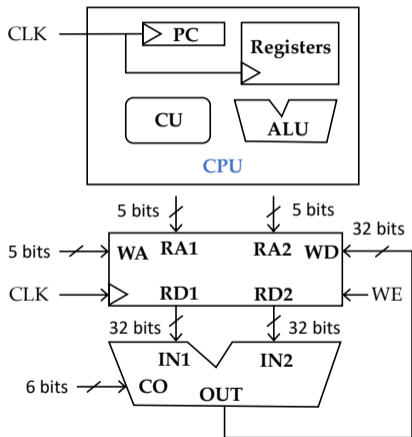

- How to wire the circuits ?

- Connect the registers with the ALU.

WA — write address

WD — write data

RA1 — read address 1

RA2 — read address 2

RD1 — read data 1

RD2 — read data 2


IN1 — input 1

IN2 — input 2

OUT — output

CO — operation

2. Arithmetic and Logical Functions

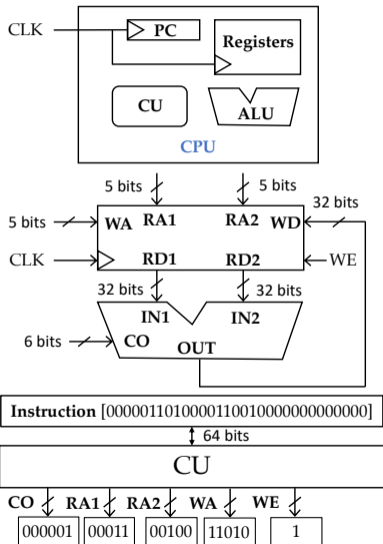

- How to wire the circuits ?


- Connect the registers with the ALU.

WA — write address WD — write data
 RA1 — read address 1 RA2 — read address 2
 RD1 — read data 1 RD2 — read data 2
 IN1 — input 1 IN2 — input 2
 OUT — output CO — operation

- Feed the CU with the input instruction, and let it output signals for CO, RA1, RA2, WA and WE.

- $R3 + R4 \Rightarrow R26$ after CLK!

2. Arithmetic and Logical Functions

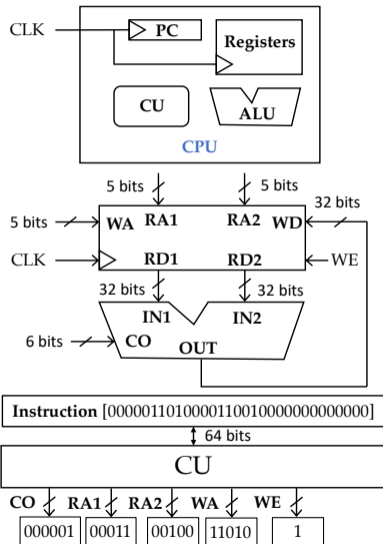

- How to wire the circuits ?


- The other instructions can be handled similarly.

CU — combinational logic


ALU — combinational logic

- Knowledge in Chapter 5 allows us to build them.


2. Arithmetic and Logical Functions

 

 - Enriching arithmetic functions by adding constants to instructions.




2. Arithmetic and Logical Functions

 

- Enriching arithmetic functions by adding constants to instructions.



 e.g., add R1 and 127, storing the results to R2.



- Useful for loading constants to registers.

$$65539 = \underbrace{0000000000000001}_{16 \text{ bits}} \underbrace{0000000000000011}_{16 \text{ bits}}$$


step1. $R3 - R3 \Rightarrow R3$ (set R3 to 0)

step3. $R3 \ll 16 \Rightarrow R3$ (set R3 to 65536)

step2. $R3 + 1 \Rightarrow R3$ (set R3 to 1)

step4. $R3 + 3 \Rightarrow R1$ (set R3 to 65539)

3. Reading and Writing Memory

 

- The instructions

Loading


$$MEM[ADDR] \Rightarrow REG$$

Storing

$$REG \Rightarrow MEM[ADDR]$$

ADDR is stored in a register.

3. Reading and Writing Memory

 

- The instructions
Loading
 $MEM[ADDR] \Rightarrow REG$
Storing
 $REG \Rightarrow MEM[ADDR]$

ADDR is stored in a register.

Let $LOAD = 31$, $STORE = 32$ for COMMAND


6 bits	5 bits	5 bits	16 bits
COMMAND	REG	ADDR	0

e.g., loading memory address stored in register R2 into register R1.

LOAD	R1	R2	0
------	----	----	---

10001	0001	0010	0000000000000000
-------	------	------	------------------

3. Reading and Writing Memory

 

Example

Loading memory address
256 to R1


$$R3 - R3 \Rightarrow R3$$

$$R3 + 256 \Rightarrow R3$$

$$MEM[R3] \Rightarrow R1$$


- Need to extend the CPU hardware to accommodate these.

Changing PC

 

➤ By default, the PC changes incrementally.

$$PC + 4 \Rightarrow PC$$

 

➤ To supporting branching and looping, we need jumping functions.

Let $JMP = 33$ if $REG = 0$, then


$$\left\{ \begin{array}{l} PC + 4 \Rightarrow MEM[R2] \\ MEM[R1] \Rightarrow PC \end{array} \right.$$

6 bits	5 bits	5 bits	5 bits	11 bits
JMP	R1	R2	REG	0

e.g., if $R3 = 0$, then jump to R1 and store old $PC + 4$ to R2.

10011	00001	00010	00011	00000000000
-------	-------	-------	-------	-------------

4. Talking to Devices

 


The principle


- Devices can send signals to the CPU to interrupt its current execution, in order to send signals (e.g., key press, mouse click).
- CPU can call devices to send signals (e.g., play sound).
- CPU talks to devices through agreed memory.
- More to discuss in OS lecture.

The Implementation

Vacuum Tube

 

Transistor

 

Integrated Circuit



Paper Tape



Floppy Disk



Keyboard and Mouse



Cloud Storage



The Implementation

- Computer Word
 - byte → 16 bits machines
 - 32 bits machines
 - 64 bits machines
- CPU Speed (In the 1950s)
 - from 1 kHz to a few hundred kHz
 - IBM 701 → around 17 kHz
- Memory (In the 1950s)
 - IBM 701 → 2048 words of 36 bits each

In the marketing of hard disk drives,
 $1K = 1000$ (*kilo*)
 $1M = 1000K \approx 1\text{million}$ (*mega*)
 $1G = 1000M$
 $1T = 1000G$
 $1P = 1000T$
 $b = \textit{bit}$, $B = \textit{byte}$